

Chapter 3


Digital Design and Computer Architecture: ARM® Edition

Sarah L. Harris and David Money Harris



Chapter 3 :: Topics

 - Introduction
- Latches and Flip-Flops
- Synchronous Logic Design
- Finite State Machines
- Timing of Sequential Logic
- Parallelism



Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has ***memory***.
- Some definitions:
 - **State**: all the information about a circuit necessary to explain its future behavior
 - **Latches and flip-flops**: state elements that store one bit of state
 - **Synchronous sequential circuits**: combinational logic followed by a bank of flip-flops



Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information





State Elements

- The state of a circuit influences its future behavior
- State elements store state
 - Bistable circuit
 - SR Latch
 - D Latch
 - D Flip-flop



Bistable Circuit

  - Fundamental building block of other state elements
- Two outputs: Q , $\bar{Q}$
- No inputs



Bistable Circuit Analysis



- Consider the two possible cases:

– $Q = 0$:

then $Q = 0, \bar{Q} = 1$ (consistent)

– $Q = 1$:

then $Q = 1, \bar{Q} = 0$ (consistent)

  


- Stores 1 bit of state in the state variable, Q (or $\bar{Q}$)
- But there are **no inputs to control the state**



SR (Set/Reset) Latch

- SR Latch

 


- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$



SR Latch Analysis


– $S = 1, R = 0$:

then $Q = 1$ and $\bar{Q} = 0$

 

– $S = 0, R = 1$:

then $Q = 0$ and $\bar{Q} = 1$

 


SR Latch Analysis

– $S = 1, R = 0$:

then $Q = 1$ and $\bar{Q} = 0$


Set the output

 

– $S = 0, R = 1$:

then $Q = 0$ and $\bar{Q} = 1$



Reset the output

 

SR Latch Analysis


– $S = 0, R = 0$:

then $Q = Q_{prev}$

  

– $S = 1, R = 1$:



then $Q = 0, \bar{Q} = 0$

 

SR Latch Analysis


– $S = 0, R = 0$:

then $Q = Q_{prev}$
Memory!

  

– $S = 1, R = 1$:

 
then $Q = 0, \bar{Q} = 0$
Invalid State
 $Q \neq \text{NOT } \bar{Q}$



SR Latch Symbol

- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S , R inputs
 - **Set:** Make the output 1 ($S = 1, R = 0, Q = 1$)
 - **Reset:** Make the output 0 ($S = 0, R = 1, Q = 0$)
- **Must do something to avoid invalid state (when $S = R = 1$)**


SR Latch
Symbol

 


D Latch

- Two inputs: CLK , D
 - CLK : controls *when* the output changes
 - D (the data input): controls *what* the output changes to
- Function
 - When $CLK = 1$,
 D passes through to Q (*transparent*)
 - When $CLK = 0$,
 Q holds its previous value (*opaque*)
- Avoids invalid case when
 $Q \neq \text{NOT } \bar{Q}$

D Latch
Symbol

 


D Latch Internal Circuit

 

CLK	D	$\overline{D}$	S	R	Q	$\overline{Q}$
0	X					
1	0					
1	1					

D Latch Internal Circuit

 


CLK	D	$\overline{D}$	S	R	Q	$\overline{Q}$
0	X	$\overline{X}$	0	0	Q_{prev}	$\overline{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0



D Flip-Flop


- **Inputs:** CLK , D
- **Function**
 - Samples D on rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK
- Called *edge-triggered*
- Activated on the clock edge

D Flip-Flop
Symbols


 


D Flip-Flop Internal Circuit


 
- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When $CLK = 0$
 - L1 is transparent
 - L2 is opaque
 - D passes through to N1
- When $CLK = 1$
 - L2 is transparent
 - L1 is opaque
 - N1 passes through to Q
- Thus, on the edge of the clock (when CLK rises from 0→1)
 - D passes through to Q




D Latch vs. D Flip-Flop

  

D Latch vs. D Flip-Flop

  


Registers: Multi-bit Flip-Flop

 

Enabled Flip-Flops

 
- **Inputs:** CLK , D , EN
 - The enable input (EN) controls when new data (D) is stored
- **Function**
 - $EN = 1$: D passes through to Q on the clock edge
 - $EN = 0$: the flip-flop retains its previous state



Resettable Flip-Flops

- **Inputs:** *CLK*, *D*, *Reset*
- **Function:**
 - **Reset = 1:** *Q* is forced to 0
 - **Reset = 0:** flip-flop behaves as ordinary D flip-flop

Symbols

 


Resettable Flip-Flops

- Two types:
 - **Synchronous:** resets at the clock edge only
 - **Asynchronous:** resets immediately when *Reset* = 1
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?



Resettable Flip-Flops

 
- Two types:
 - **Synchronous:** resets at the clock edge only
 - **Asynchronous:** resets immediately when $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?



Settable Flip-Flops



- Inputs: CLK , D , Set
- Function:
 - $Set = 1$: Q is set to 1
 - $Set = 0$: the flip-flop behaves as ordinary D flip-flop

Symbols

 


Sequential Logic

  - Sequential circuits: all circuits that aren't combinational
- A problematic circuit:




Sequential Logic

 - Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



 - No inputs and 1-3 outputs
- Astable circuit, oscillates
- Period depends on inverter delay
- It has a **cyclic path**: output fed back to input




Synchronous Sequential Logic Design

- Breaks cyclic paths by **inserting registers**
- Registers contain **state** of the system
- State changes at clock edge: system **synchronized** to the clock
- **Rules** of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock signal
 - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
 - Finite State Machines (FSMs)
 - Pipelines



Finite State Machine (FSM)

 
- Consists of:
 - **State register**
 - Stores current state
 - Loads next state at clock edge
 - **Combinational logic**
 - Computes the next state
 - Computes the outputs




Finite State Machines (FSMs)

- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 - **Moore FSM**: outputs depend only on current state
 - **Mealy FSM**: outputs depend on current state *and* inputs

Moore FSM

 


Mealy FSM

 


FSM Example

 - Traffic light controller
 - Traffic sensors: T_A , T_B (TRUE when there's traffic)
 - Lights: L_A , L_B




FSM Black Box

 - **Inputs:** CLK , $Reset$, T_A , T_B
- **Outputs:** L_A , L_B




FSM State Transition Diagram

 - **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Diagram

 - **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Table

Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	



FSM State Transition Table

Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0



FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11



FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$



FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0				
0	1				
1	0				
1	1				

Output	Encoding
green	00
yellow	01
red	10



FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

$$L_{A1} = S_1$$

$$L_{A0} = \bar{S}_1 S_0$$


$$L_{B1} = \bar{S}_1$$

$$L_{B0} = S_1 S_0$$


Output	Encoding
green	00
yellow	01
red	10




FSM Schematic: State Register

 



FSM Schematic: Next State Logic

 

FSM Schematic: Output Logic

 

FSM Timing Diagram

  


FSM State Encoding

- **Binary** encoding:
 - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
 - One state bit per state
 - Only one state bit HIGH at once
 - i.e., for 4 states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic is simpler




Moore vs. Mealy FSM

 - Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design Moore and Mealy FSMs of the snail's brain.




State Transition Diagrams

Moore FSM

 

Mealy FSM

 

Mealy FSM: arcs indicate input/output

Moore FSM State Transition Table

Current State		Inputs	Next State	
s_1	s_0		s'_1	s'_0
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		

State	Encoding
S0	00
S1	01
S2	10



Moore FSM State Transition Table

Current State		Inputs	Next State	
S_1	S_0		S'_1	S'_0
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

State	Encoding
S0	00
S1	01
S2	10

$$S'_1 = S_0 A$$

$$S'_0 = \overline{A}$$



Moore FSM Output Table

Current State		Output
s_1	s_0	Y
0	0	
0	1	
1	0	



Moore FSM Output Table

Current State		Output
S_1	S_0	Y
0	0	0
0	1	0
1	0	1

$$Y = S_1$$



Mealy FSM State Transition & Output Table

Current State	Input	Next State	Output
S_0	A	S'_0	Y
0	0		
0	1		
1	0		
1	1		

State	Encoding
S0	00
S1	01



Mealy FSM State Transition & Output Table

Current State	Input	Next State	Output
S_0	A	S'_0	Y
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1


State	Encoding
S0	00
S1	01

$$S'_0 = \overline{A}$$


$$Y = S_0 A$$




Moore FSM Schematic

 

Mealy FSM Schematic

 

Moore & Mealy Timing Diagram

 


Factoring State Machines

- Break complex FSMs into smaller interacting FSMs
- Example: Modify traffic light controller to have Parade Mode.
 - Two more inputs: P , R
 - When $P = 1$, enter Parade Mode & Bravado Blvd light stays green
 - When $R = 1$, leave Parade Mode




Parade FSM


Unfactored FSM

 


Factored FSM

 


Unfactored FSM

 

Factored FSM

 

Lights FSM

 

Mode FSM

FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
 - a. Rewrite state transition table with state encodings
 - b. Write output table
5. For a Mealy machine:

Rewrite combined state transition and output table with state encodings
6. Write Boolean equations for next state and output logic
7. Sketch the circuit schematic




Timing

- Flip-flop samples D at clock edge
- D must be stable when sampled
- Similar to a photograph, D must be stable around clock edge
- If not, metastability can occur




Input Timing Constraints

 - **Setup time:** t_{setup} = time *before* clock edge data must be stable (i.e. not changing)
- **Hold time:** t_{hold} = time *after* clock edge data must be stable
- **Aperture time:** t_a = time *around* clock edge data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)



Output Timing Constraints

 - **Propagation delay:** t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- **Contamination delay:** t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)




Dynamic Discipline

- Synchronous sequential circuit inputs must be stable during aperture (setup and hold) time around clock edge
- Specifically, inputs must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge




Dynamic Discipline

 - The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements



Setup Time Constraint

 
- Depends on the **maximum** delay from register R1 through combinational logic to R2
- The input to register R2 must be stable at least t_{setup} before clock edge



$$T_c \geq$$

Setup Time Constraint

 - Depends on the **maximum** delay from register R1 through combinational logic to R2
- The input to register R2 must be stable at least t_{setup} before clock edge




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$



Setup Time Constraint

 - Depends on the **maximum** delay from register R1 through combinational logic to R2
- The input to register R2 must be stable at least t_{setup} before clock edge




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

$(t_{pcq} + t_{\text{setup}})$: sequencing overhead



Hold Time Constraint

 
- Depends on the **minimum** delay from register R1 through the combinational logic to R2
- The input to register R2 must be stable for at least t_{hold} after the clock edge



$$t_{\text{hold}} <$$

Hold Time Constraint

 
- Depends on the **minimum** delay from register R1 through the combinational logic to R2
- The input to register R2 must be stable for at least t_{hold} after the clock edge



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

Hold Time Constraint

 
- Depends on the **minimum** delay from register R1 through the combinational logic to R2
- The input to register R2 must be stable for at least t_{hold} after the clock edge



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq ?$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate


$$\left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$



Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Hold time constraint:


$$t_{ccq} + t_{cd} > t_{hold} ?$$

$(30 + 25) \text{ ps} > 70 \text{ ps}$? **No!**



Timing Analysis

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq ?$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$



Timing Analysis

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right]$$

Hold time constraint:


$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$




Clock Skew

 - The clock doesn't arrive at all registers at same time
- **Skew**: difference between two clock edges
- Perform **worst case analysis** to guarantee dynamic discipline is not violated for any register – many registers in a system!



Setup Time Constraint with Skew

 - In the worst case, CLK2 is earlier than CLK1




$$T_c - t_{skew} \geq t_{pcq} + t_{pd} + t_{setup}$$



Setup Time Constraint with Skew

 - In the worst case, CLK2 is earlier than CLK1




$$T_c - t_{skew} \geq t_{pcq} + t_{pd} + t_{setup}$$

$$T_c \geq ?$$

Setup Time Constraint with Skew

 - In the worst case, CLK2 is earlier than CLK1




$$T_c - t_{skew} \geq t_{pcq} + t_{pd} + t_{setup}$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

Setup Time Constraint with Skew

 - In the worst case, CLK2 is earlier than CLK1




$$T_c - t_{skew} \geq t_{pcq} + t_{pd} + t_{setup}$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$


Hold Time Constraint with Skew

 - In the worst case, CLK2 is later than CLK1



Hold Time Constraint with Skew

 - In the worst case, CLK2 is later than CLK1




$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$



Hold Time Constraint with Skew

 - In the worst case, CLK2 is later than CLK1





$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$

$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$


Violating the Dynamic Discipline

  Asynchronous (for example, user) **inputs** might violate the dynamic discipline




Metastability

 - **Bistable devices:** two stable states, and a metastable state between them
- **Flip-flop:** two stable states (1 and 0) and one metastable state
- If flip-flop lands in metastable state, could stay there for an undetermined amount of time



Flip-Flop Internals

 - Flip-flop has **feedback**: if Q is somewhere between 1 and 0, cross-coupled gates drive output to either rail (1 or 0)



- Metastable signal**: if it hasn't resolved to 1 or 0
- If flip-flop input changes at random time, **probability that output Q is metastable** after waiting some time, t :

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

t_{res} : time to resolve to 1 or 0

T_0, τ : properties of the circuit



Metastability

- **Intuitively:**

T_0/T_c : probability input changes at a bad time (during aperture)

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

τ : time constant for how fast flip-flop moves away from metastability


$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- If flip-flop samples metastable input, if you wait long enough (t), the output will have resolved to 1 or 0 with high probability.




Synchronizers

 - **Asynchronous inputs are inevitable** (user interfaces, systems with different clocks interacting, etc.)
- **Synchronizer goal:** make the probability of failure (the output Q still being metastable) low
- Synchronizer cannot make the probability of failure 0



Synchronizer Internals

 
- Synchronizer: built with two back-to-back flip-flops
- Suppose D is transitioning when sampled by F1
- Internal signal D2 has $(T_c - t_{\text{setup}})$ time to resolve to 1 or 0



Synchronizer Probability of Failure

For each sample, probability of failure is:
 
$$P(\text{failure}) = (T_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$



Synchronizer Mean Time Between Failures

- If asynchronous input changes once per second, probability of failure per second is $P(\text{failure})$.
- If input changes N times per second, probability of failure per second is:


$$P(\text{failure})/\text{second} = (NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

- Synchronizer fails, on average, $1/[P(\text{failure})/\text{second}]$
- Called *mean time between failures*, MTBF:

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] = (T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$




Example Synchronizer

 

- Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$ $\tau = 200 \text{ ps}$
 $T_0 = 150 \text{ ps}$ $t_{\text{setup}} = 100 \text{ ps}$
 $N = 10 \text{ events per second}$
- What is the probability of failure? MTBF?



Example Synchronizer

 

- Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$ $\tau = 200 \text{ ps}$
 $T_0 = 150 \text{ ps}$ $t_{\text{setup}} = 100 \text{ ps}$
 $N = 10 \text{ events per second}$
- What is the probability of failure? MTBF?

$$P(\text{failure}) = (150 \text{ ps} / 2 \text{ ns}) e^{-(1.9 \text{ ns}) / 200 \text{ ps}}$$
$$= 5.6 \times 10^{-6}$$

$$P(\text{failure})/\text{second} = 10 \times (5.6 \times 10^{-6})$$
$$= 5.6 \times 10^{-5} / \text{second}$$

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] \approx 5 \text{ hours}$$



Parallelism

- **Two types of parallelism:**
 - **Spatial parallelism**
 - duplicate hardware performs multiple tasks at once
 - **Temporal parallelism**
 - task is broken into multiple stages
 - also called pipelining
 - for example, an assembly line



Parallelism Definitions

- **Token:** Group of inputs processed to produce group of outputs
- **Latency:** Time for one token to pass from start to end
- **Throughput:** Number of tokens produced per unit time

Parallelism increases throughput



Parallelism Example

- Ben Bitdiddle bakes cookies to celebrate traffic light controller installation
 - 5 minutes to roll cookies
 - 15 minutes to bake
- What is the latency and throughput without parallelism?



Parallelism Example

- Ben Bitdiddle bakes cookies to celebrate traffic light controller installation
 - 5 minutes to roll cookies
 - 15 minutes to bake
- What is the latency and throughput without parallelism?

Latency = 5 + 15 = 20 minutes = **1/3 hour**

Throughput = 1 tray/ 1/3 hour = **3 trays/hour**




Parallelism Example

- What is the latency and throughput if Ben uses parallelism?
 - **Spatial parallelism:** Ben asks Allysa P. Hacker to help, using her own oven
 - **Temporal parallelism:**
 - two stages: rolling and baking
 - He uses two trays
 - While first batch is baking, he rolls the second batch, etc.



Spatial Parallelism

 


Latency = ?

Throughput = ?



Spatial Parallelism

 


Latency = 5 + 15 = 20 minutes = **1/3 hour**

Throughput = 2 trays/ 1/3 hour = **6 trays/hour**



Temporal Parallelism

 


Latency = ?

Throughput = ?



Temporal Parallelism

 

Latency = 5 + 15 = 20 minutes = **1/3 hour**

Throughput = 1 trays/ 1/4 hour = **4 trays/hour**

Using both techniques, the throughput would be **8 trays/hour**

